


Assignment - 6

Muhammed Erkmen

Question1


This circuit is a communication circuit which uses UART. It has receiver (RX) and transmitter (TX) modules. Input is 8 bit length data and output is as input.

RTL Schematic:

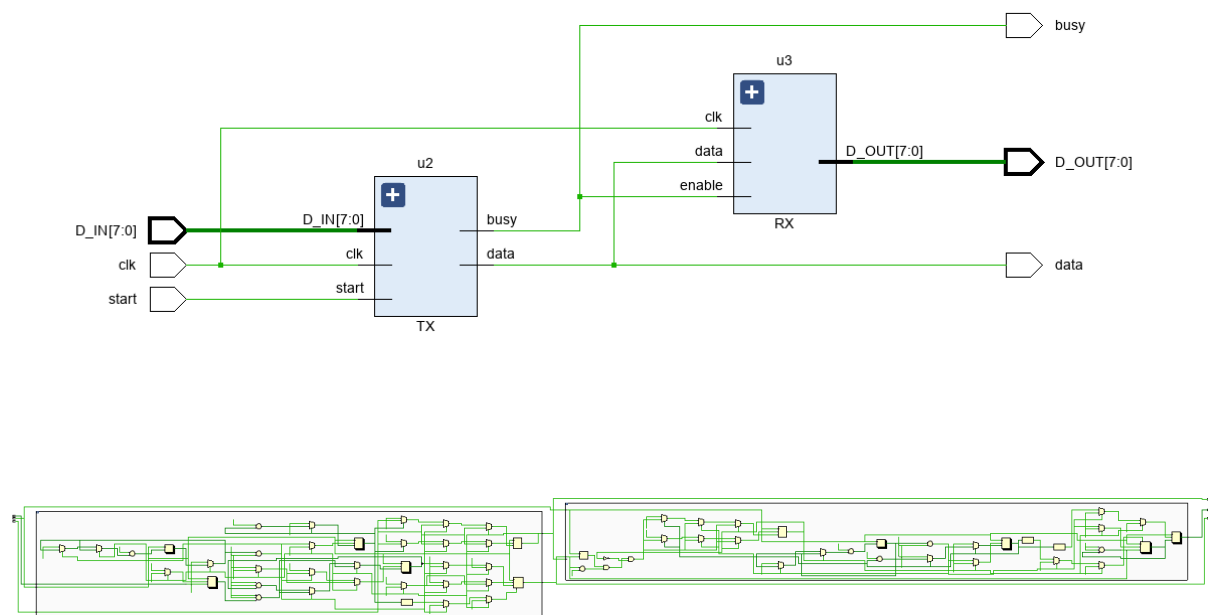

Testbench results:

 As it seems from testbench results, data transmitter and data receiver behaves correctly.



Timing Report:

Timing		Setup	Hold	Pulse Width
Worst Negative Slack (WNS):	-1.159 ns			
Total Negative Slack (TNS):	-11.223 ns			
Number of Failing Endpoints:	10			
Total Number of Endpoints:	127			
Implemented Timing Report				

Utilization Reports:

Name	Slice LUTs (303600)	Slice Registers (607200)	Slice (75900)	LUT as Logic (303600)	Bonded IOB (600)	BUFGCTRL (32)
question1	54	66	23	54	20	1
u2 (TX)	31	33	12	31	0	0
u3 (RX)	23	33	11	23	0	0


Name	Slice LUTs (303600)	Slice Registers (607200)	Slice (75900)	LUT as Logic (303600)	Bonded IOB (600)	BUFGCTRL (32)
question1	0.02%	0.01%	0.03%	0.02%	3.33%	3.13%
u2 (TX)	0.01%	<0.01%	0.02%	0.01%	0.00%	0.00%
u3 (RX)	<0.01%	<0.01%	0.01%	<0.01%	0.00%	0.00%

Question2:


In this question, i connected my fifo and rx-tx modules together. Used RX to get data from keyboard and wrote these datas to the FIFO. FIFO has a read button and i can read the ASCII code of the keyboard input from leds. When FIFO is empty, TX sends an 'e' signal to the computer. When FIFO is full, TX sends a 'f' signal to the computer.

I choosed 115.200

RTL Schematic

 

 As it seems in the testbench, when FIFO reaches full, TX input changes to 'f' and sends just 1 "f" signal to the computer.




For T = 8ns, timing report:

Fmax = 109.122MHz

Timing	Setup Hold Pulse Width
Worst Negative Slack (WNS):	-1.164 ns
Total Negative Slack (TNS):	-11.449 ns
Number of Failing Endpoints:	10
Total Number of Endpoints:	299
Implemented Timing Report	

Utilization Report:

 

Utilization

Post-Synthesis | Post-Implementation

Graph | Table

Resource	Utilization	Available	Utilization %
LUT	101	303600	0.03
FF	157	607200	0.03
IO	14	600	2.33
BUFG	1	32	3.13

PIN PLAN

[illegible]