


Muhammed Erkmen

## Assignment – 4


This assignment wants a 2-64 bit input 128bit output multiplier.

Question1:

Simulation results

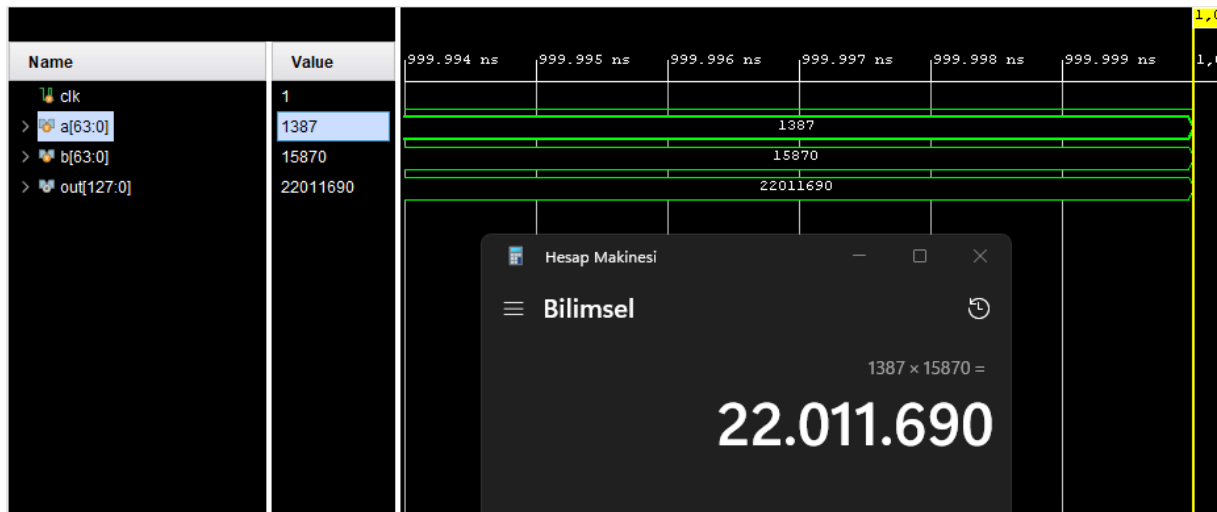

RTL Schematic

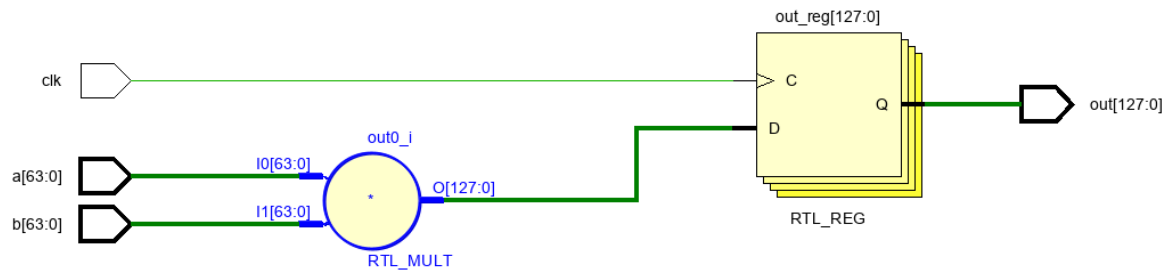

### Design Timing Summary

Setup	Hold	Pulse Width
Worst Negative Slack (WNS): -2,246 ns	Worst Hold Slack (WHS): 0,866 ns	Worst Pulse Width Slack (WPWS): 4,600 ns
Total Negative Slack (TNS): -337,059 ns	Total Hold Slack (THS): 0,000 ns	Total Pulse Width Negative Slack (TPWS): 0,000 ns
Number of Failing Endpoints: 276	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0
Total Number of Endpoints: 400	Total Number of Endpoints: 400	Total Number of Endpoints: 273



Timing constraints are not met.

Maximum Operation Frequency is  $1/(T-WNS) = (10^9)/(12,246)$

Fmax = 81,65931 MHz.
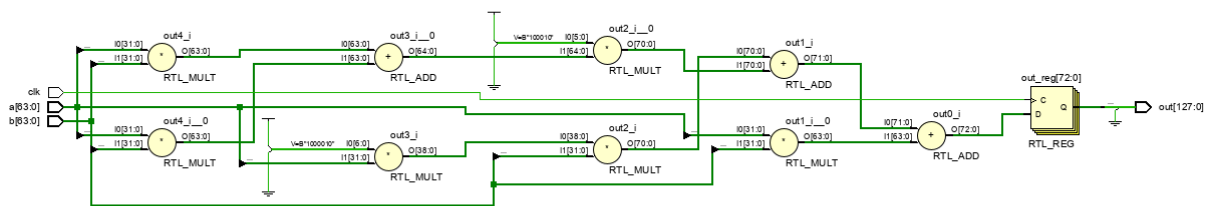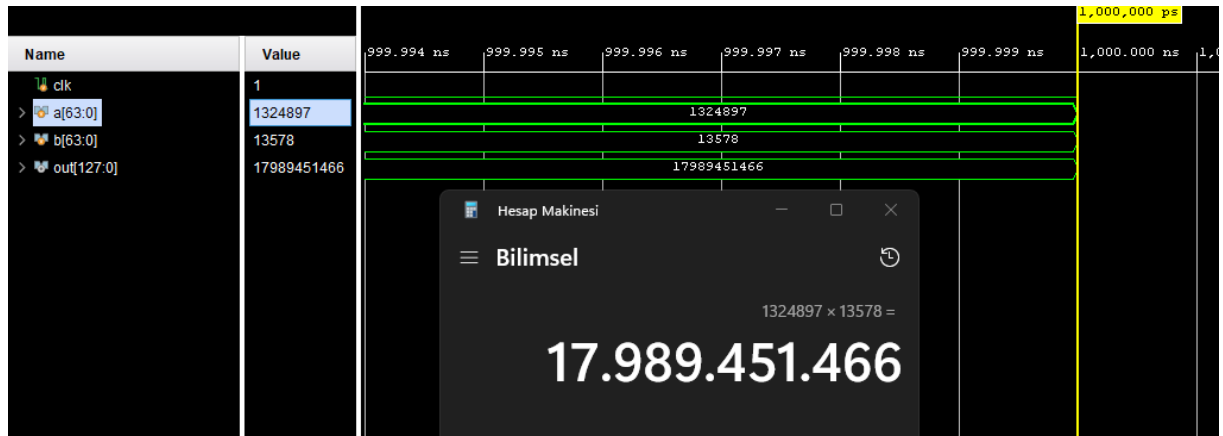
## Question2

In this part, karatsuba algorithm has been used to make multiplication faster.



### Design Timing Summary

Setup	Hold	Pulse Width
Worst Negative Slack (WNS): -0,983 ns	Worst Hold Slack (WHS): 0,339 ns	Worst Pulse Width Slack (WPWS): 4,650 ns
Total Negative Slack (TNS): -18,933 ns	Total Hold Slack (THS): 0,000 ns	Total Pulse Width Negative Slack (TPWS): 0,000 ns
Number of Failing Endpoints: 39	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0
Total Number of Endpoints: 146	Total Number of Endpoints: 146	Total Number of Endpoints: 74



Timing constraints are not met.

$$\text{Max Operation Frequency} = 1/(\text{Ts} - \text{WNS})$$

$$\text{Fmax} = 91,0498 \text{ MHz}$$
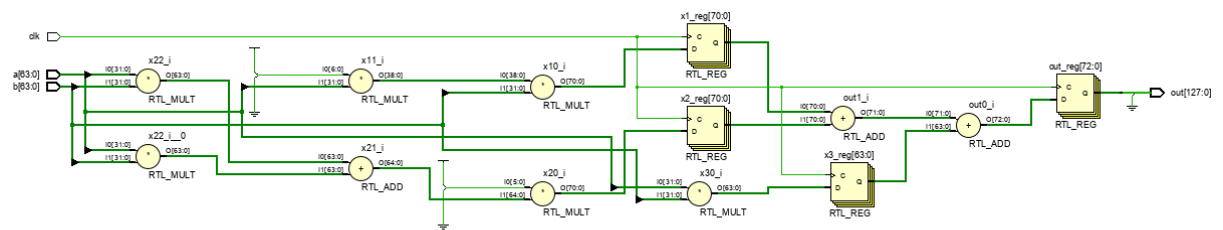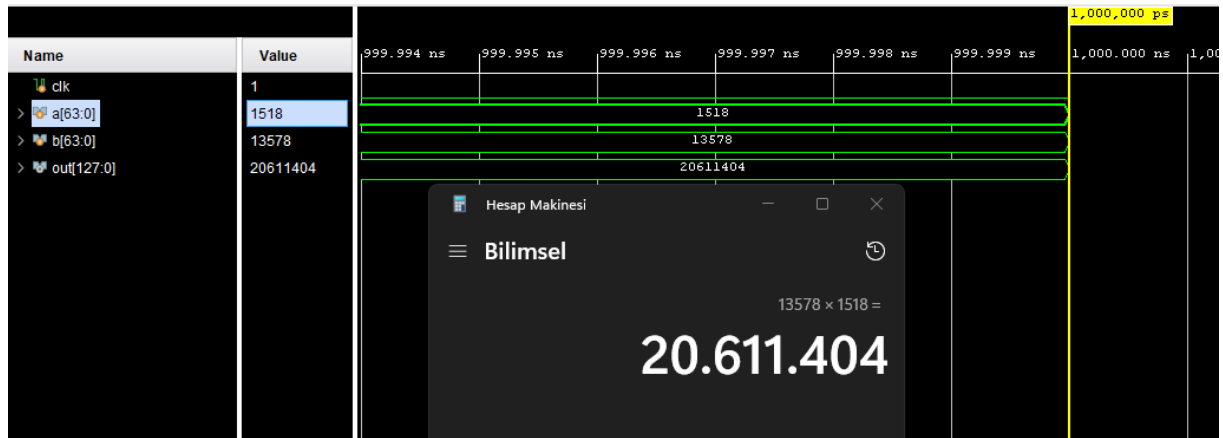
### Question 3

In this question, i divided the operations to 3 parts with using pipelines. Kept results in 3 different registers and than calculated the output in another register.



#### Design Timing Summary

Setup	Hold	Pulse Width
Worst Negative Slack (WNS): -2,539 ns	Worst Hold Slack (WHS): 0,092 ns	Worst Pulse Width Slack (WPWS): 3,100 ns
Total Negative Slack (TNS): -268,135 ns	Total Hold Slack (THS): 0,000 ns	Total Pulse Width Negative Slack (TPWS): 0,000 ns
Number of Failing Endpoints: 214	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0
Total Number of Endpoints: 584	Total Number of Endpoints: 584	Total Number of Endpoints: 216

Timing constraints are not met.

$$F_{max} = 1/(T - WNS) = 1/7 - (-2.539) = 104.832 \text{ MHz}$$

Application	Clock Period	WNS	Fmax
* operator	10nS	-2.246	81.659 MHz
Karatsuba	10nS	-0.983	91.0498
Karatsuba & Pipeline	7nS	-2.539	104.832 MHz